



## **MURANG'A UNIVERSITY COLLEGE**

*( A Constituent College of Jomo Kenyatta University of Agriculture and Technology)*

**DEPARTMENT:** ELECTRICAL ENGINEERING  
**LEVEL:** DIPLOMA  
**CLASS:** MRUC/ME/P/14DS  
**TERM/SEMESTER:** I1  
**ACADEMIC YEAR:** 2014/2015  
**UNIT:** ELECTRICAL SCIENCE II  
**UNIT CODE:** SEM 1202  
**TIME:** 2 HOURS  
**DATE:** 21<sup>ST</sup> AUGUST 2015

### ***Instructions to candidates***

This paper contains four (4) questions

Question 1 is compulsory

Answer any other 2 questions

You should have the following for this examination;

- Drawing instruments
- Scientific calculator

Mobile Phones Not Allowed In Exam Room

1. (a) Define the following terms:
- i. Unidirectional waveform
  - ii. Alternating waveform
  - iii. Period, T.
  - iv. Frequency
  - v. Amplitude
  - vi. Instantaneous value
  - vii. Peak-to-peak value **(7marks)**
- (b) An alternating current completes 5 cycles in 8ms. Determine its frequency? **(3marks)**
- (c) An alternating voltage is given by  $V = 75\sin(200\pi t - 0.25)$  volts. Find:
- (i) The periodic time, T
  - (ii) The peak-to-peak value
  - (iii) The r.m.s value
  - (iv) The phase angle in degrees and minutes relative to  $75\sin 200\pi t$ . **(10marks)**
- (d) The current in a.c circuit at any time  $t$  seconds is given by  
 $i = 120\sin(100\pi t + 0.36)$  amperes  
 Find:  
 The peak value, the periodic time, the frequency and phase angle relative to  $120\sin 100\pi t$ . **(10marks)**
2. (a) Determine the capacitive reactance of a capacitor of  $10\mu\text{F}$  when connected to a Circuit of frequency 20 kHz. **(2marks)**
- (b) A coil of inductance  $159.2\text{mH}$  and resistance  $20\Omega$  is connected in series with a  $60\Omega$  resistor to a  $240\text{V}$ ,  $50\text{Hz}$  supply. Determine:
- i. The impedance of the circuit
  - ii. The current in the circuit
  - iii. The circuit phase current
  - iv. The potential difference across the  $60\Omega$  resistor **(12marks)**
- (c) Describe the following moving-iron instrument with aid of labelled diagrams.
- (i) Attraction type
  - (ii) Repulsion **(6marks)**
3. (a) Define the term Q – factor. **(2marks)**
- (b) A capacitor C is connected in series with a  $40\Omega$  resistor across a supply voltage of frequency  $60\text{Hz}$ . A current of  $3\text{A}$  flows and the circuit impedance is  $50\Omega$ . Calculate:
- (i) The value of the capacitance, C.
  - (ii) The supply voltage
  - (iii) The phase angle between the supply voltage and current
  - (iv) The potential difference across the resistor
  - (v) The potential difference across the capacitor
  - (vi) Draw the phasor diagram **(18 marks)**

4. (a). A 5KVA single phase transformer has turns ratio of 10:1 and is fed from a 2.5KV supply. Neglecting losses, determine ;
- (i) The full load secondary current
  - (ii) Minimum load current which can be connected across the secondary winding to give full load KVA
  - (iii) The primary current at full load KVA. **(12marks)**
- (b) Describe the construction and principle of operation of a transformer with an aid of diagram. **(8marks)**