



MERU UNIVERSITY OF SCIENCE AND TECHNOLOGY

P.O. Box 972-60200 – Meru-Kenya.

Tel: 020-2069349, 061-2309217. 064-30320 Cell phone: +254 712524293, +254 789151411

Fax: 064-30321

Website: www.must.ac.ke Email: info@must.ac.ke

University Examinations 2013/2014

THIRD YEAR, SECOND SEMESTER EXAMINATION FOR DIPLOMA IN ELECTRICAL
ENGINEERING

EEE 0246: ELEMENTS OF ELECTRICAL POWER SYSTEMS III

DATE: APRIL 2014

TIME: 1 ½ HOURS

INSTRUCTIONS: Answer question *one* and any other *two* questions

QUESTION ONE – (30 MARKS)

- (a) Describe a protective system. (3 Marks)
- (b) Describe three qualities of a protective system. (6 Marks)
- (c) With the aid of a sketch describe the shaded pole as used in protection. (6 Marks)
- (d) A 5000KVA, 6 600V, star connected alternator has a synchronous reactance of 20ohms per phase and 0.5ohm resistance. It is protected by a merzt price balanced current system which operates when out of balance current exceed, 30% of load current. Determine what proportion of alternator winding is unprotected if the star point is earthed through a resistance of 6.5ohms. (10 Marks)
- (e) Describe differential protection. (3 Marks)
- (f) Explain what is meant by I.D.M.T relay in power protection. (2 Marks)

QUESTION TWO – (15 MARKS)

- (a) With the aid of a diagram describe Bulcholz transfer protection. (7 Marks)
- (b) With the aid of a diagram explain differential protection of generators. (6 Marks)
- (c) State two types of protection. (2 Marks)

QUESTION THREE – (15 MARKS)

- (a) Describe the following terms as used in protection
- (i) Pick up current
 - (ii) Current setting
 - (iii) Graded time protection
 - (iv) Distance/time protection (4 Marks)
- (b) The neutral point of a three phase 20mVA, 11KV alternator is earthed through a resistance of 5 ohms, the relay is set to operate when there is an out of balance current of 1.5A. The C.T have a ratio of 1000/5. What is the percentage of winding protected? Also calculate the earthing resistance required to protect 90% of the winding. (9 Marks)
- (c) Describe the operation of electromagnetic relay as used in protection. (2 Marks)

QUESTION FOUR – (15 MARKS)

- (a) With the aid of a diagram describe time-distance impedance relay. (6 Marks)
- (b) Briefly explain the function of the following device in a protective system. (6 Marks)
- (i) Protective relay
 - (ii) Circuit breaker
 - (iii) Current transformer
- (c) Describe the principle of mertz price protection. (3 Marks)