



TECHNICAL UNIVERISTRY OF MOMBASA

Faculty of Engineering & Technology

DEPARTMENT OF COMPUTER SCIENCE & INFORMATION TECHNOLOGY

UNIVERSITY EXAMINATION FOR DEGREE IN:
BACHELOR OF SCIENCE IN INFORMATION TECHNOLOGY
(BSIT 14S – Y1 S1)

ICS 2200: ELECTRONICS

END OF SEMESTER EXAMINATION
SERIES: DECEMBER 2014
TIME: 2 HOURS

Instructions to Candidates:

You should have the following for this examination

- *Answer Booklet*

This paper consists of **FIVE** questions. Attempt question **ONE (Compulsory)** and any other **TWO** questions
Maximum marks for each part of a question are as shown

This paper consists of **TWO** printed pages

Question One (Compulsory)

- a) (i) Define capacitor. (2 marks)
(ii) Describe any FOUR types of inductors (8 marks)
- b) Describe any TWO major groups of electronic circuits (4 marks)
- c) Describe any THREE popular ways of connecting resistors together with the aid of a sketch. (6 marks)
- d) Explain any EIGHT important characteristics of PN junction diode (4 marks)
- e) (i) Define operations Amplifiers (2 marks)

(ii) Describe any TWO major applications of operational amplifier

(4 marks)

Question Two

Discuss the operation and application of summing operational amplifier with the aid of a sketch.

(20 marks)

Question Three

Distinguish between Depletion Mode MOSFET and Enhanced Mode Channel MOSFET with the aid of a sketch. Pay attention to the V-I characteristic and symbols

(20 marks)

Question Four

Given the following diagram:

24V

a) Calculate the current through R2 using either Thevenin's theorem or Norton's Theorem **(14 marks)**

b) Justify your answer using Kirchhoff's Law of current and voltage

(6 marks)

Question Five

a) Describe any FIVE types of diodes

(10 marks)

b) Describe any TWO applications of diodes in power rectification with the aid of a sketch

(4 marks)

c) Describe any THREE classes of transistor Amplifier Operation with the aid of a sketch.

(6 marks)