



**MURANG'A UNIVERSITY COLLEGE**  
*(A Constituent College of Jomo Kenyatta University of Agriculture and Technology)*

**SCHOOL OF COMPUTING AND INFORMATION TECHNOLOGY**

**DEPARTMENT OF INFORMATION TECHNOLOGY**

**MAIN EXAMINATION**

**LEVEL:** DIPLOMA

**CLASS:** DIT14SEPT

**TERM/SEMESTER:** II

**ACADEMIC YEAR:** 2014/2015

**UNIT:** BASIC ELECTRONICS

**UNIT CODE:** SCI 1109

**TIME:** 2 HOURS

***Instructions to candidates:***

This paper contains **FOUR (4)** questions.

Answer **QUESTION ONE** and **ANY OTHER TWO** questions.

You should have the following for this examination;

- Answer booklet
- Scientific calculator

**NB: NO MOBILE PHONES ALLOWED IN THE EXAMINATION ROOM.**

**Section A****QUESTION ONE (compulsory)**

- (a) Distinguish between conductors and semi-conductors. **(2 marks)**
- (b) Using well labelled diagrams distinguish between the three bipolar transistor configurations. **(6 marks)**
- (c) Name two types of MOSFETs. **(4 marks)**
- (d) Calculate the equivalent resistance of four resistors of  $4\Omega$ ,  $6\Omega$ ,  $8m\Omega$  and  $10M\Omega$  connected in parallel. **(4 marks)**
- (e) Using biasing circuits, briefly explain the following:
- Forward bias
  - Reverse bias **(8 marks)**
- (f) Using appropriate diagrams, explain the formation of p-type semi-conductor materials through the process of doping. **(6 marks)**

**Section B****QUESTION TWO**

- (a) Use the energy band theory to distinguish between conductors, semi-conductors and insulators **(12 marks)**
- (b) Name the two materials commonly used to make semiconductor materials. **(2 marks)**
- (c) Determine the range of values expected for a resistor with colour coding: red-black-brown-green-silver. **(6 marks)**

**QUESTION THREE**

- (a) Capacitances of  $2\mu\text{F}$ ,  $7\mu\text{F}$ ,  $11\mu\text{F}$  and  $16\mu\text{F}$  are connected in series to a direct voltage supply of 120 V. Determine:
- The equivalent circuit capacitance
  - The total charge
  - The charge on the  $2\mu\text{F}$  capacitor. **(7 marks)**
- (b) Show that the equivalent resistance for three resistors connected in parallel is given by:  
 $C_{eq} = C_1 + C_2 + C_3$  **(5 marks)**
- (c) Define the following terms as used in semiconductor theory:
- Hole
  - Diffusion
  - Hall effect
  - Carrier lifetime **(8 marks)**

**QUESTION FOUR**

- (a) Determine the voltage drop across a resistor of  $7\text{M}\Omega$  when a current of 3 mA is passed through it. **(4 marks)**
- (b) Sketch a well labelled V-I characteristic curve of a PN-junction diode. **(6 marks)**
- (c) Using standard symbols distinguish between NPN and PNP transistors. **(4 marks)**
- (d) Define the following terms:
- Knee voltage
  - Peak-Inverse voltage
  - Maximum power rating **(6 marks)**