



MURANG'A UNIVERSITY COLLEGE
(A Constituent College of Jomo Kenyatta University of Agriculture and Technology)

DEPARTMENT: ELECTRICAL ENGINEERING

LEVEL: DIPLOMA

CLASS: KNEC/EEP/15DJ3

MODULE: III

ACADEMIC YEAR: 2014/15

TERM: I

UNIT: POWER ELECTRONICS

UNIT CODE: EE1307

DATE: 27TH APRIL 2015

TIME: 2 HOURS

Instructions to candidates

This paper contains seven (7) Questions

Attempt any five (5) questions

You should have the following for this examination;

- Drawing instruments
- Scientific calculator

➤ **NO MOBILE PHONES ARE ALLOWED WITHIN THE EXAMINATION ROOM!!!!!!**

QUESTION 1: (20 marks)

- (a). Briefly explain the reverse recovery characteristics of a diode including the effects of reverse recovery time and the cause of the reverse recovery time in a *pn*-junction. [4mrks]
- (b). i). Draw the typical *v-i* characteristics of thyristors [2mrks]

ii). Label v, i , reverse breakdown voltage, forward break-over voltage, forward leakage current, reverse leakage current, forward voltage drop, holding current and latching current. [4mrks]

(c). If the converter of the figure below has a purely resistive load of R and the delay angle is $\alpha = \pi/2$, determine the following: (i) the efficiency, (ii) the form factor FF , (iii) the ripple factor RF , (iv) the transformer utilization factor TUF and (v) the peak inverse voltage PIV . [8mrks]

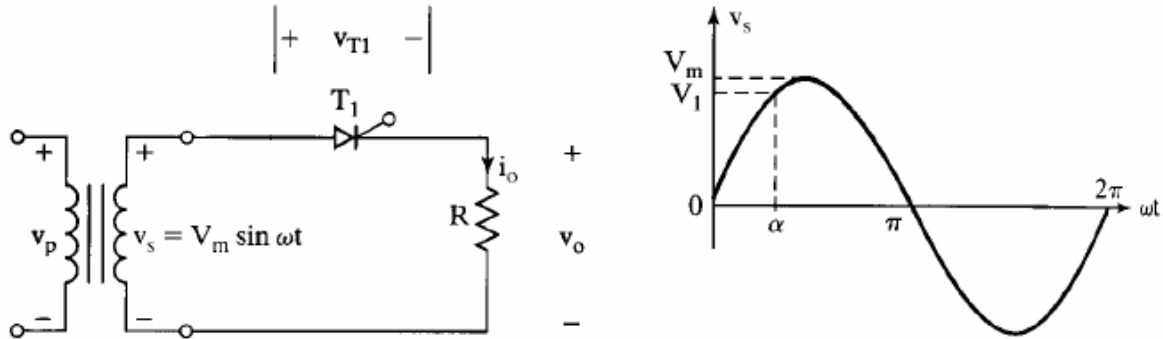


Figure 1

(d). Explain the working principle of single phase cycloconverter with circuit diagram and waveforms [2mrks]

Question 2 (20 marks)

(a). A three phase full converter bridge is connected to a 3-phase 400V, 50Hz supply having a source inductance of 5mH. The total current is constant at 20A. If the load consists of a dc voltage source of 400V, having an internal resistance of 1Ω, calculate the firing angle α and overlap angle μ for this condition. [8mrks]

(b). List two methods of voltage control employed in ac voltage controllers. [2mrks]

(c). Draw the power circuitry for a single-phase fully controlled converter and explain its operation with relevant waveforms. Derive the expression for average load voltage assuming continuous current operation. [10mrks]

QUESTION 3: (20 marks)

(a). For a single phase ac voltage controller feeding a resistive load, draw the waveforms of source voltage, gating angle, output voltage, source and output currents and voltage across the SCRs. Describe its working with reference to the waveforms drawn. [10mrks]

(b). An ac voltage regulator operating from 230V, 50Hz supply uses integral cycle control to control the flow of power to 10Ω load. The thyristors conduct for 18 cycles and remain off for 32 cycles.

Find

- (i). rms value of output voltage
- (ii). power output to the load
- (iii). power input to the regulator
- (iv). input power factor
- (v). average and rms values of SCR current (neglect losses). **[10mrks]**

QUESTION 4: (20 marks)

- (a). Draw the circuit of a dc chopper with RL load and explain its operation with waveforms. **[6mrks]**
- (b). A step down dc chopper is connected to a resistive load of 30Ω . The dc supply voltage is 200V. The duty ratio of the chopper is 0.8 with a chopping frequency of 400Hz. Determine the average load voltage, average load current and ON time of the chopper. **[6mrks]**
- (c). A buck-boost converter is to supply a maximum power of 75 W at -50 V from a 40 V dc source. The output voltage ripple must be no more than 1%. The switching frequency f_s is 40kHz. Assume that the converter operates at the boundary of continuous/discontinuous conduction mode when 75W is supplied.
 - (i). Calculate the duty cycle D .
 - (ii). Calculate the required size of the inductance L and capacitance C .
 - (iii). Determine the average, maximum and minimum inductor currents.
 - (iv). Sketch the diode current waveform and find its average value. **[8mrks]**

Question 5: (20 marks)

- (a). List the commonly used PWM technique for voltage and waveform control of inverters and explain any one of methods in detail. **[6mrks]**
- (b). Draw the power circuitry for IGBT based single-phase bridge inverter and explain its operation with relevant waveforms. **[4mrks]**
- (c). A three-phase bridge inverter is fed from a dc source of 200V. if the load is star connected with 20Ω resistance phase obtain the value of
 - (i) rms load current
 - (ii) rms current rating of thyristors
 - (iii) The load power for 120° conduction and 180° conduction **[10mrks]**

Question 6 (20 marks)

- (a). Highlight the two main classification of thyristor commutation. **[2mrks]**
- (b). With the aid of relevant circuit diagrams and wave forms, explain the principle used in resonant pulse commutation of SCRs. **[6mrks]**
- (c). Explain the operation of a single-phase half controlled bridge converter with R-L load and derive the load voltage and load current for a firing angle, $\alpha = 20^\circ$. Draw schematic diagram with relevant wave forms. **[12mrks]**

Question 7 (20 marks)

- (a). A three phase half controlled converter is operated from a 3 phase star connected 220V 50Hz supply and the load is 10Ω . If the average output voltage is 25% of the maximum possible average output voltage, calculate:
- i) Output d.c. voltage
 - ii) Output d.c. current
 - iii) Rectifier efficiency
 - iv) Transformer utilization factor (TUF) **[8mrks]**
- (b). With the aid of a circuit and waveforms diagrams, explain the principles of a cycloconverter with and intergroup reactor working in the circulating current mode **[10mrks]**
- (c). List any two power electronic circuits that use source voltage for thyristor commutation **[2mrks]**