



MASENO UNIVERSITY
UNIVERSITY EXAMINATIONS 2015/2016

**FIRST YEAR FIRST SEMESTER EXAMINATION FOR THE DEGREE OF
BACHELOR OF SCIENCE IN COMPUTER SCIENCE**

MAIN CAMPUS

CCT 115: ENGINEERING DRAWING

Date: 18th January, 2016

Time: 11.00 - 1.00pm

INSTRUCTIONS:

- **Answer Question ONE and any other TWO Questions**
- **Diagrams, where required should be clearly drawn and labeled.**
- **Mobile phones are strictly forbidden in this exam.**

Question One (Compulsory 30marks)

- a) What is graphic communication? 2marks
- b) Discuss the two basic types of drawing. 4marks
- c) Explain the Purpose of Technical drawing. 4marks
- d) Explain the different application of technical drawing 6marks
- e) Define a Title Block and give some of its features? 5marks
- f) Define projection 3marks
- g) The two broad types of projections, both with several sub classifications, are parallel projection and perspective projection. Discuss. 6marks

Question Two (20 marks)


- a) Mention any eight main drawing equipments 4marks
- b) Explain the use of the different drawing equipments mentioned above 8marks
- c) Discuss the different type of pencils with their use 4marks
- d) Explain the purpose and theory of multi view projections 4marks

Question Three (20 marks)

- a) Define Orthographic projection. Describe "Glass box method" of orthographic first and third angle projections based on the technical drawing procedure. 10marks
- b) Discuss the purpose of dimensioning 4marks
- c) Explain the difference among dimension line, extension line and leaders 6marks

Question Four (20 marks)

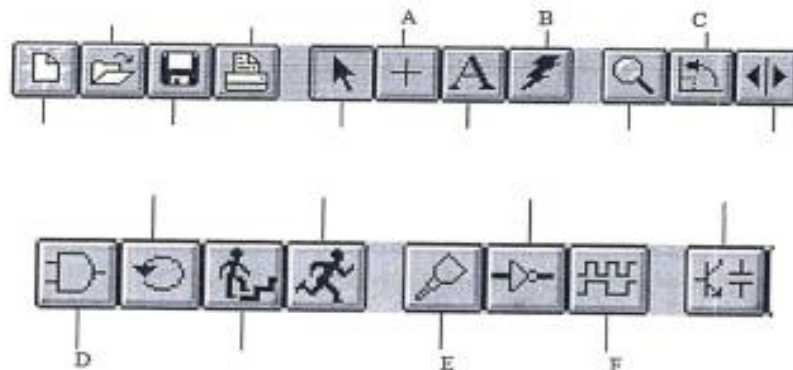
- a) The figure below shows part of circuit maker toolbar. Identify and briefly describe the function of tool A, B, C, D, E and F on the Toolbar shown. 6marks



- b) Circuit Maker is a computer aided software that is used for schematic drawing and simulation of digital and analog electronic circuits. What do you understand by the terms: 4marks
 - i. Schematic Drawing
 - ii. Simulation of electronic circuits.
 - iii. Digital circuits
 - iv. Analog circuits

c) Why do you think it is always necessary to simulate electronic circuits first before transferring the design to a real Print Circuit Board (PCB)? 4marks

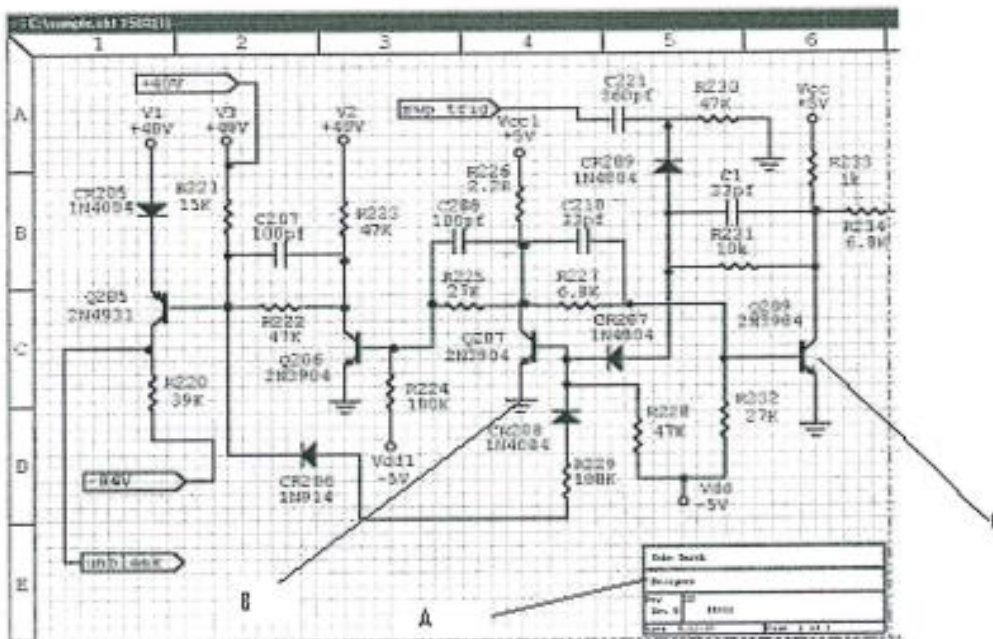d) Name any possible four features found in part A. State the significance of each feature. 4marks



Question Five (20 marks)


- a) Identify and explain the function of the circuit maker CAD software buttons marked A,B,C,D.

4marks



- b) The figure below is a 12V to 5V dc-dc converter circuit diagram. Explain how you would design and simulate the circuit schematic in Circuit Maker.

6marks

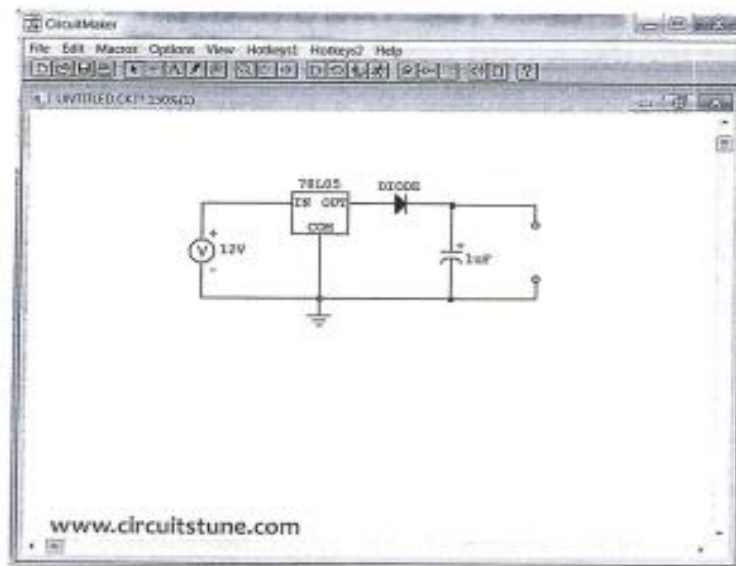

- c) Fill in the truth-table for all the gates listed below. Create a circuit using CircuitMaker for one of these gates to determine its truth table experimentally so as to see that it agrees with what you had filled out on the truth-table. Those gates with the letter n in them (NAND, NOR,XNOR)

have a NOT gate(inverter) on their output. For example a NAND gate is an AND gate with a NOT on its output. 10marks

p	q	p and q	p or q	p nand q	p nor q	p xor q	p xnor q
0	0						
0	1						
1	0						
1	1						